```
`timescale 1ns / 1ps
// Company:
// Engineer:
// Create Date: 11/07/2018 03:52:05 PM
// Design Name:
// Module Name: StateMachine
// Project Name:
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
module StateMachine(
   input clk,
   input btnC,
   input btnU,
   input btnD,
   input TimeUp,
   input lastled,
   output ShowTime,
   output LoadTime,
   output RunTime,
   output IncU,
   output IncD,
   output ShowScore,
   output FlashU,
   output FlashD,
   output shift
   );
   wire[11:0] D, Q;
   wire enable = 1'b1;
   wire btnCsyn,btnDsyn,btnUsyn;
   assign btnCsyn = btnC;
   assign btnDsyn = btnD;
   assign btnUsyn = btnU;
```

```
FDRE #(.INIT(1'b0)) syc0 (.C(clk), .CE(enable), .D(btnC), .Q(btnCsyn));
      FDRE #(.INIT(1'b0)) syc1 (.C(clk), .CE(enable), .D(btnD), .Q(btnDsyn));
      FDRE #(.INIT(1'b0)) syc2 (.C(clk), .CE(enable), .D(btnU), .Q(btnUsyn));
//
    //Idle
    assign D[0] = Q[0] \& \text{btnCsyn} \mid Q[2] \& \text{TimeUp} \& \text{btnDsyn} \& \text{btnUsyn};
    FDRE \#(.INIT(1'b1)) t0 (.C(clk), .CE(enable), .D(D[0]), .Q(Q[0]));
    //wait
    assign D[1] = Q[11] \mid Q[1] \& \text{-lastled};
    FDRE \#(.INIT(1'b0)) t1 (.C(clk), .CE(enable), .D(D[1]), .Q(Q[1]));
    //Accp
    assign D[2] = Q[2] \& -btnUsyn\& -btnDsyn\& -TimeUp | Q[1] \& lastled;
    FDRE \#(.INIT(1'b0)) t2 (.C(clk), .CE(enable), .D(D[2]), .Q(Q[2]));
    //TIE
    assign D[3] = Q[2] \& \neg TimeUp \& btnDsyn \& btnUsyn;
    FDRE \# (.INIT(1'b0)) t3 (.C(clk), .CE(enable), .D(D[3]), .Q(Q[3]));
    //UFirst
    assign D[4] = Q[2] & \text{TimeUp} & \text{btnDsyn} & \text{btnUsyn} | Q[4] & \text{TimeUp} & \text{btnDsyn};
    FDRE \#(.INIT(1'b0)) t4 (.C(clk), .CE(enable), .D(D[4]), .Q(Q[4]));
    //Dfirst
    assign D[5] = Q[2] \& \text{TimeUp} \& \text{btnDsyn} \& \text{-btnUsyn} | Q[5] \& \text{TimeUp} \& \text{-btnUsyn};
    FDRE \#(.INIT(1'b0)) t5 (.C(clk), .CE(enable), .D(D[5]), .Q(Q[5]));
    //Uwin
    assign D[6] = Q[5] \& \text{TimeUp} \& \text{btnUsyn} \mid Q[4] \& \text{TimeUp} \& \text{-btnDsyn};
    FDRE \#(.INIT(1'b0)) t6 (.C(clk), .CE(enable), .D(D[6]), .Q(Q[6]));
    //Dwin
    assign D[7] = Q[4] & \text{TimeUp} & \text{btnDsyn} \mid Q[5] & \text{TimeUp} & \text{btnUsyn};
    FDRE \#(.INIT(1'b0)) t7 (.C(clk), .CE(enable), .D(D[7]), .Q(Q[7]));
    //UFlash
    assign D[8] = Q[6] \mid Q[8] \& \text{-btnCsyn};
    FDRE \#(.INIT(1'b0)) t8 (.C(clk), .CE(enable), .D(D[8]), .Q(Q[8]));
    //Dflash
    assign D[9] = Q[7] | Q[9] \& \text{-btnCsyn};
    FDRE \#(.INIT(1'b0)) t9 (.C(clk), .CE(enable), .D(D[9]), .Q(Q[9]));
    //Tflash
```

//

//

```
assign D[10] = Q[3] | Q[10]&~btnCsyn;
FDRE #(.INIT(1'b0)) t10 (.C(clk), .CE(enable), .D(D[10]), .Q(Q[10]));

//Load
   assign D[11] = (Q[0]|Q[8]|Q[9]|Q[10])&btnCsyn;
   FDRE #(.INIT(1'b0)) t11 (.C(clk), .CE(enable), .D(D[11]), .Q(Q[11]));

assign ShowTime = Q[1];
assign LoadTime = Q[11];
assign RunTime = Q[2]| Q[4]| Q[5];
assign IncU = Q[3]| Q[6];
assign IncD = Q[3]| Q[6];
assign ShowScore = Q[0]| Q[8]| Q[9]| Q[10];
assign FlashU = Q[8]| Q[10];
assign FlashD = Q[9]| Q[10];
assign shift = Q[1];
```

endmodule